
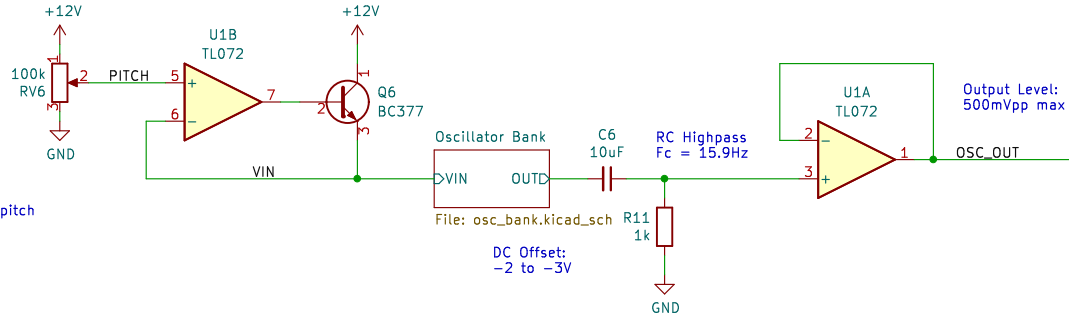


OSCILLATORS



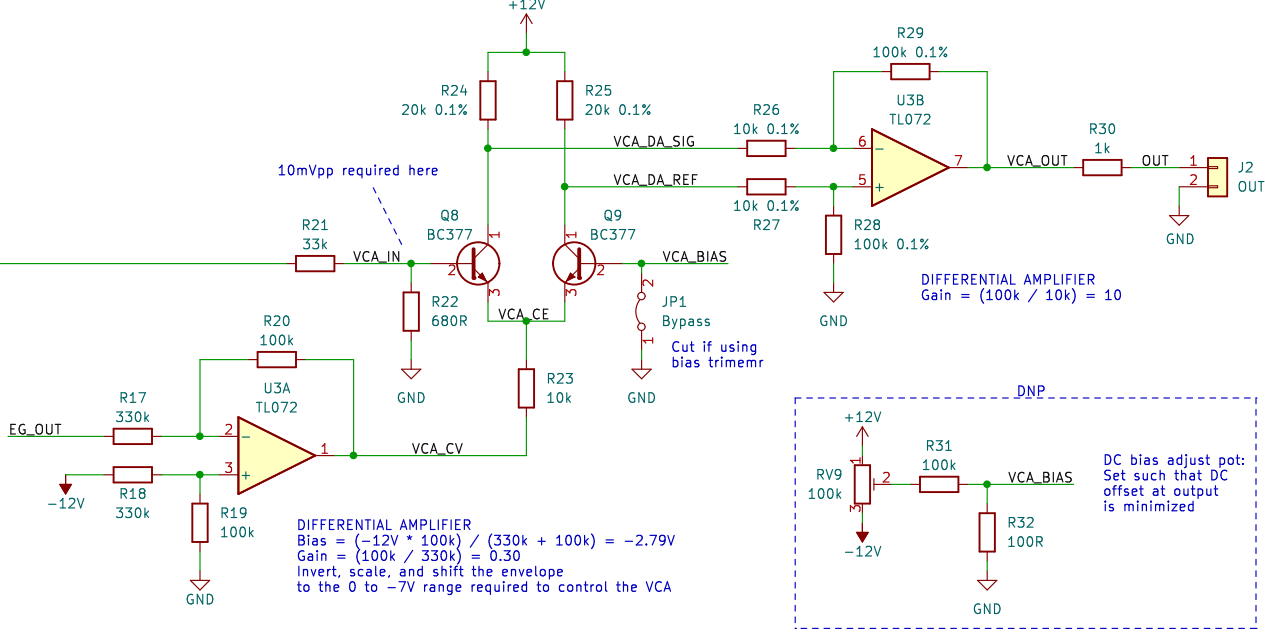
Summing Amplifier
Gain = -1
Produces a negative voltage
current sink for the oscillators
Higher voltage difference -> higher pitch




VOLTAGE CONTROLLED AMPLIFIER




AR ENVELOPE GENERATOR

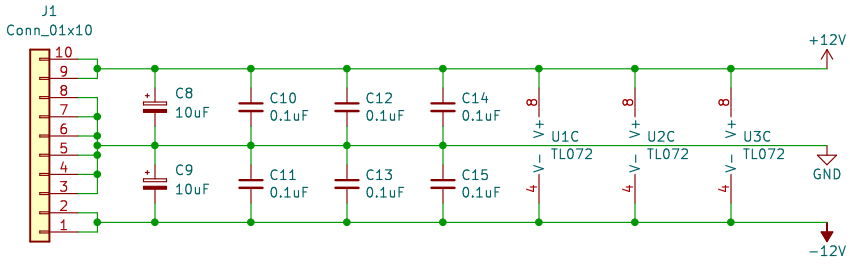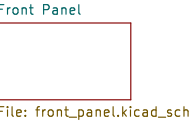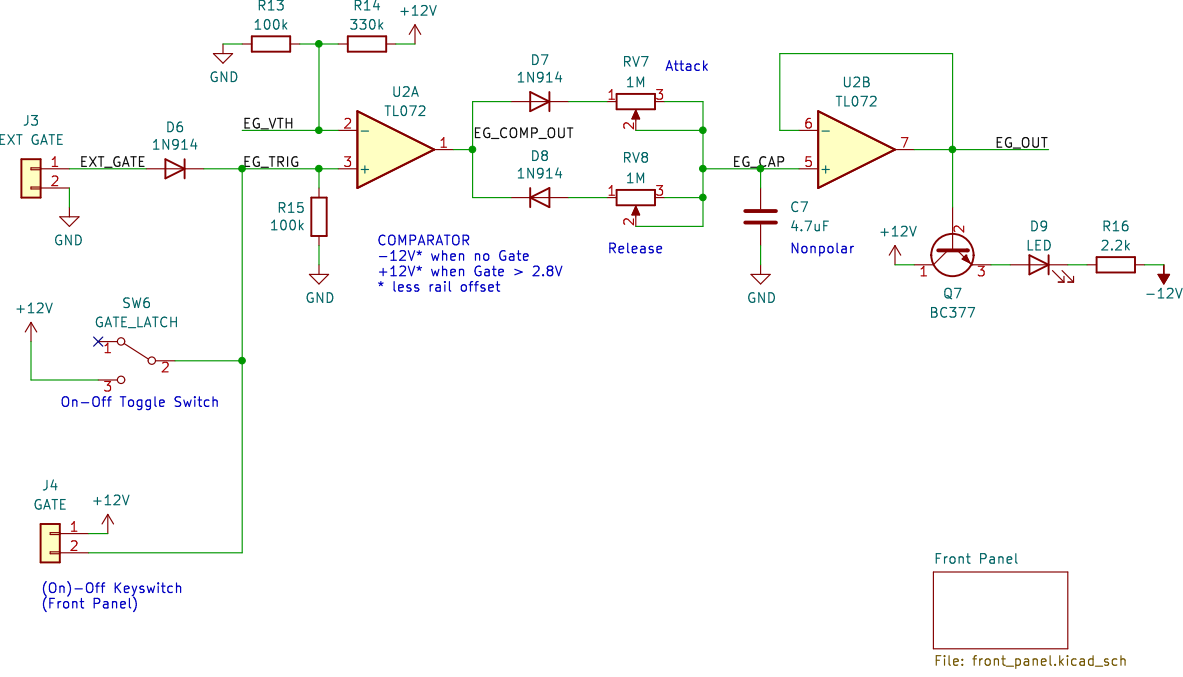

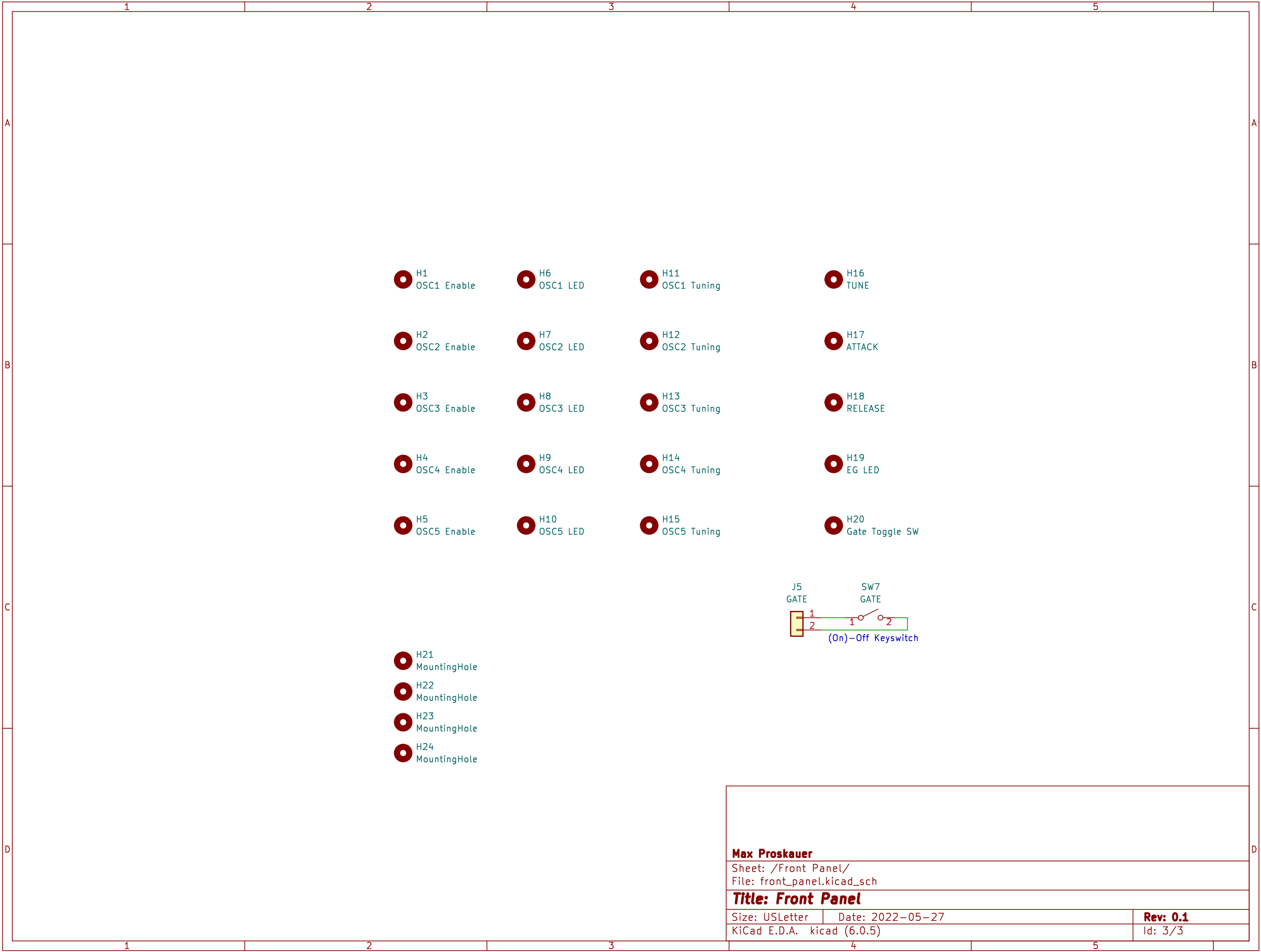

REVERSE AVALANCHE OSCILLATORS

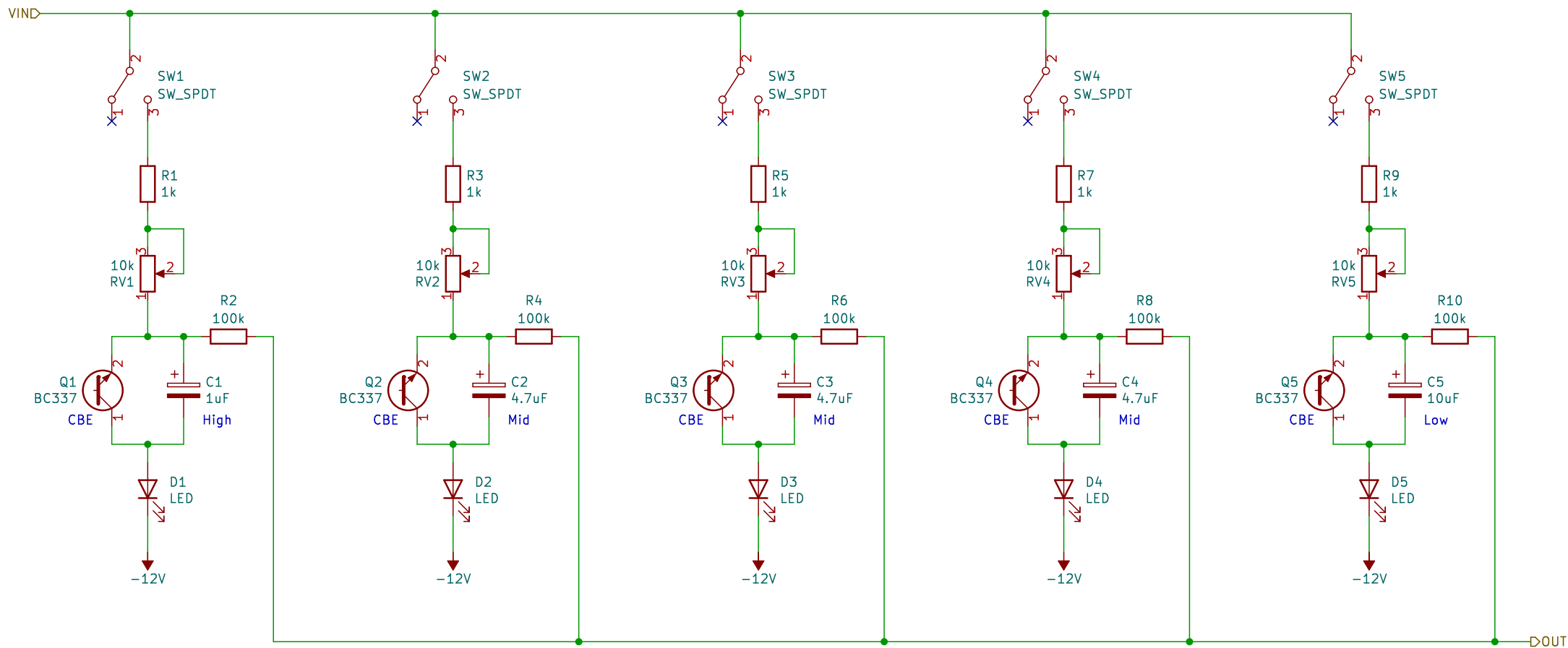

Remember:
It's not out of tune;
It's microtonal.